



---

**119 PHYS**

**Experiment Title:**

**Name:**

**ID number:**

**Section:**

**E-mail:**

**Group members:**

**Lab instructor: Saja Algessair**

1-Objective:

2-Theory:

3-Equipment:

4-Precaution:

5-Analyze:

1. Series circuits:

<b>V (.....)</b>	<b>I (.....)</b>

2. Parallel circuits:

<b>V (.....)</b>	<b>I (.....)</b>

6- Calculation:

7- Conclusion: